

# MEEC/MIEEC

## ELECTRONICS FOR MICRO-SYSTEMS

---

### Lab#1 A Temperature Meter System with 3 Sensors, Relay and GUI

---

**Authors:**

Martim Duarte Agostinho (70392)

Lorem Ipsum ( $\text{ISTID} \in \mathbb{Z}^+$ )

Sofia Margarida Mafra Dias Inácio (58079)

[md.agostinho@campus.fct.unl.pt](mailto:md.agostinho@campus.fct.unl.pt)

[lorem.ipsum@campus.fct.unl.pt](mailto:lorem.ipsum@campus.fct.unl.pt)

[sm.inacio@campus.fct.unl.pt](mailto:sm.inacio@campus.fct.unl.pt)

# Contents


<b>1</b>	<b>Introduction</b>	<b>3</b>
<b>2</b>	<b>Temperature Sensors</b>	<b>4</b>
2.1	NTC - Negative Temperature Coefficient . . . . .	4
2.2	LM35 - Precision Centigrade Temperature Sensor . . . . .	4
2.3	DS18B20 - Digital Thermometer . . . . .	4
<b>3</b>	<b>System Design</b>	<b>4</b>
3.1	Analog FrontEnd (AFE) NTC . . . . .	4
3.2	LM35 . . . . .	6
3.3	DS18B20 ??(Este tem Dimensionamento?) . . . . .	6
3.4	Relé de saída . . . . .	6
<b>4</b>	<b>Simulations</b>	<b>6</b>
<b>5</b>	<b>Implementation and Experimental Tests</b>	<b>6</b>
<b>6</b>	<b>Results Analysis</b>	<b>6</b>
<b>7</b>	<b>Conclusion</b>	<b>6</b>

## List of Figures

1	Temperature sensing system with 3 three types of sensors. . . . .	3
2	AFE for the LM35 sensor. . . . .	4
3	AFE error curve. . . . .	4
4	NTC voltage divider. . . . .	5

# 1 Introduction

explain the requirements and the main objectives of the project Se calhar dizer aqui quais sao as metricas por onde podemos avaliar a nossa solucao Linearidade de output para conseguir aproveitar melhor a resolucao do adc Consumo erro

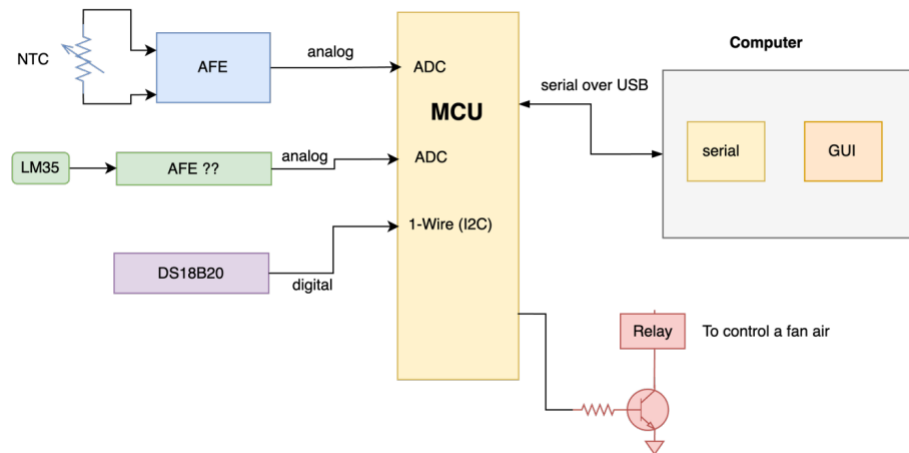


**Figure 1:** Temperature sensing system with 3 three types of sensors.


## 2 Temperature Sensors

### 2.1 NTC - Negative Temperature Coefficient

### 2.2 LM35 - Precision Centigrade Temperature Sensor

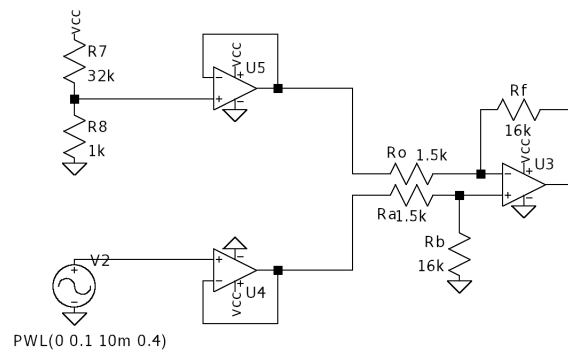

**Figure 2:** AFE for the LM35 sensor.

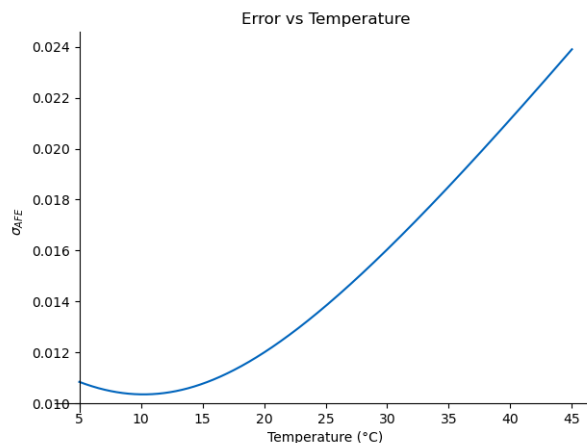

**Figure 3:** AFE error curve.

### 2.3 DS18B20 - Digital Thermometer

## 3 System Design

### 3.1 Analog FrontEnd (AFE) NTC

A parte onde definimos o intervalo de temperatura nao devia estar aqui pq é para todos os circuitos

In order to design the *NTF AFE* first it's necessary to define the temperature interval in which this circuit will work, thus it was define as  $T \in [10^{\circ}; 40^{\circ}]$ . Through the *NTC*'s datasheet the interval of its resistance values is  $R_{NTC} \in [5,282k ; 19,98k]$

For an accurate reading of the temperature it was used the *Steinhart-Hart equation*.

$$\frac{1}{T} = A + B \cdot \ln(R_{NTC}) + C \cdot [\ln(R_{NTC})]^3 \quad (1)$$


In order to find the parameters  $A$ ,  $B$  and  $C$ , its necessary to use 3 points from the datasheet. The points chosen were the two extremes and the middles point.

$$\begin{cases} R(283, 15) = 1,998 \cdot 10^4 \Omega \\ R(298, 15) = 10^4 \Omega \\ R(313, 15) = 0,5282 \cdot 10^4 \Omega \end{cases} \Leftrightarrow \begin{cases} A = 1,2 \cdot 10^{-3} \\ B = 2,1 \cdot 10^{-4} \\ C = 1,3 \cdot 10^{-7} \end{cases} \quad (2)$$

Para poder dimensionar o AFE do NTC primeiro é necessario definir o intervalo de temperaturas em que o circuito irá operar. Foi então decidido que seria adequado um temperatura  $T \in [10^\circ; 40^\circ]$ . E pelo datasheet do NTC foi obtido o intervalo da sua resistencia  $R_{NTC} \in [5,282k ; 19,98k]$

Para usar equacao Steinhart-Hart  $\frac{1}{T} = A + B \cdot \ln(R) + C \cdot [\ln(R)]^3$ , precisamos de usar 3 pontos para encontrar as constantes  $A$ ,  $B$  e  $C$ .  $R(T) = R_{NTC}$  onde  $T$  é a temperatura em kelvin e  $R_{NTC}$  é o valor da resistencia do thermistor NTC

The simplest way to convert the resistance to voltage, is to use a voltage divider circuit.

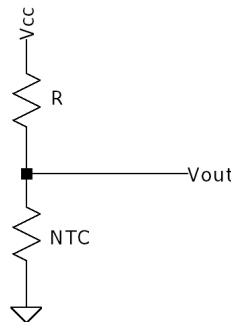

**Figure 4:** NTC voltage divider.

This approach has a few problems:

- The output resistance is really high  $R \parallel NTC$ ,
- The output voltage is highly non linear, which is a problem because this way some ADC resolution is lost.

The first problem is solved through a buffer at the entrance of the AFE, and the second is somewhat mitigated by using a resistor  $R \gg NTC$ , because, as seen in the equation a value for  $R$  will lead to small variation in the output voltage, making it closer to a straight curve.

aqui acho que se vê pela segunda derivada, quanto menor a segunda derivada mais reta é a curva certo ??

With  $R = \dots$  the output signal is  $V_{out} \in [\dots]$ . But the ADC as resolution of 12 bits and a voltage range of 3.3V, meaning that to have the best resolution possible the signal needs an offset and a gain of ... and ... respectively. This is achieved using a differential amplifier.

### 3.2 LM35

This integrated-circuit temperature sensor, generates an output voltage linearly proportional to the Centigrade temperature

$$V_{out} = 10^{-2} \cdot T$$

Thus in the specified conditions  $V_{out} \in [0.1; 0.4]$ , as done in the last section we will be using a differential amplifier to fit this interval in the *ADC*'s range.

### 3.3 DS18B20 ??(Este tem Dimensionamento?)

### 3.4 Relé de saída

## 4 Simulations

## 5 Implementation and Experimental Tests

## 6 Results Analysis

## 7 Conclusion