

MEEC/MIEEC

ELECTRONICS FOR MICRO-SYSTEMS

Lab#1 P1 A Temperature Meter System with 3 Sensors, Relay and GUI

Authors:

Martim Duarte Agostinho (70392)
Francisco Simões Coelho Sá da Costa (70386)
Sofia Margarida Mafra Dias Inácio (58079)

md.agostinho@campus.fct.unl.pt
fsc.costa@campus.fct.unl.pt
sm.inacio@campus.fct.unl.pt

Contents

1	Introduction	3
2	Temperature Sensors	4
2.1	NTC - Negative Temperature Coefficient	4
2.2	LM35 - Precision Centigrade Temperature Sensor	4
2.3	DS18B20 - Digital Thermometer	4
3	System Design	4
3.1	Analog FrontEnd (AFE) NTC	4
3.2	LM35	6
3.3	DS18B20 ??(Este tem Dimensionamento?)	6
3.4	Relé de saída	6
4	Simulations	6
5	Implementation and Experimental Tests	6
6	Results Analysis	6
7	Conclusion	6

List of Figures

1	Temperature sensing system with 3 three types of sensors.	3
2	AFE for the LM35 sensor.	4
3	AFE error curve.	4
4	NTC voltage divider.	5

1 Introduction

explain the requirements and the main objectives of the project Se calhar dizer aqui quais sao as metricas por onde podemos avaliar a nossa solucao Linearidade de output para conseguir aproveitar melhor a resolucao do adc Consumo erro

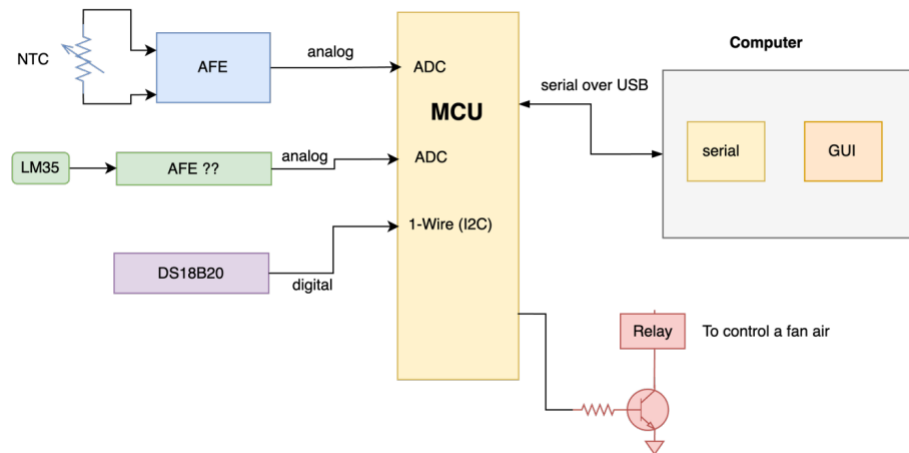


Figure 1: Temperature sensing system with 3 three types of sensors.

2 Temperature Sensors

2.1 NTC - Negative Temperature Coefficient

2.2 LM35 - Precision Centigrade Temperature Sensor

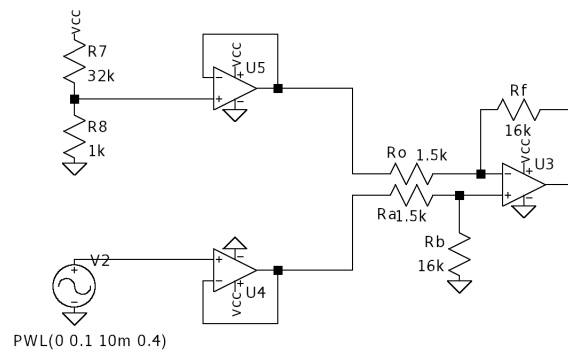


Figure 2: AFE for the LM35 sensor.

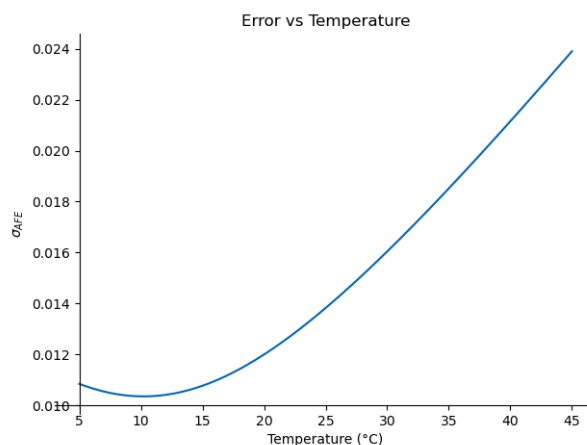


Figure 3: AFE error curve.

2.3 DS18B20 - Digital Thermometer

3 System Design

3.1 Analog FrontEnd (AFE) NTC

A parte onde definimos o intervalo de temperatura nao devia estar aqui pq é para todos os circuitos

In order to design the *NTF AFE* first it's necessary to define the temperature interval in which this circuit will work, thus it was define as $T \in [10^{\circ}; 40^{\circ}]$. Through the *NTC*'s datasheet the interval of its resistance values is $R_{NTC} \in [5, 282k ; 19, 98k]$

For an accurate reading of the temperature it was used the *Steinhart-Hart equation*.

$$\frac{1}{T} = A + B \cdot \ln(R_{NTC}) + C \cdot [\ln(R_{NTC})]^3 \quad (1)$$

In order to find the parameters A , B and C , its necessary to use 3 points from the datasheet. The points chosen were the two extremes and the middles point.

$$\begin{cases} R(283, 15) = 1,998 \cdot 10^4 \Omega \\ R(298, 15) = 10^4 \Omega \\ R(313, 15) = 0,5282 \cdot 10^4 \Omega \end{cases} \Leftrightarrow \begin{cases} A = 1,2 \cdot 10^{-3} \\ B = 2,1 \cdot 10^{-4} \\ C = 1,3 \cdot 10^{-7} \end{cases} \quad (2)$$

Para poder dimensionar o AFE do NTC primeiro é necessario definir o intervalo de temperaturas em que o circuito irá operar. Foi então decidido que seria adequado um temperatura $T \in [10^\circ; 40^\circ]$. E pelo datasheet do NTC foi obtido o intervalo da sua resistencia $R_{NTC} \in [5,282k ; 19,98k]$

Para usar equacao Steinhart-Hart $\frac{1}{T} = A + B \cdot \ln(R) + C \cdot [\ln(R)]^3$, precisamos de usar 3 pontos para encontrar as constantes A , B e C . $R(T) = R_{NTC}$ onde T é a temperatura em kelvin e R_{NTC} é o valor da resistencia do thermistor NTC

The simplest way to convert the resistance to voltage, is to use a voltage divider circuit.

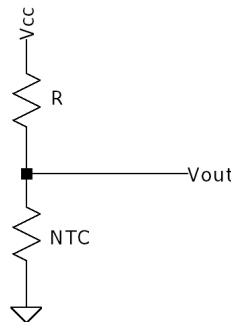


Figure 4: NTC voltage divider.

This approach has a few problems:

- The output resistance is really high $R \parallel NTC$,
- The output voltage is highly non linear, which is a problem because this way some ADC resolution is lost.

The first problem is solved through a buffer at the entrance of the AFE, and the second is somewhat mitigated by using a resistor $R \gg NTC$, because, as seen in the equation a value for R will lead to small variation in the output voltage, making it closer to a straight curve.

aqui acho que se vê pela segunda derivada, quanto menor a segunda derivada mais reta é a curva certo ??

With $R = \dots$ the output signal is $V_{out} \in [\dots]$. But the ADC as resolution of 12 bits and a voltage range of 3.3V, meaning that to have the best resolution possible the signal needs an offset and a gain of ... and ... respectively. This is achieved using a differential amplifier.

3.2 LM35

This integrated-circuit temperature sensor, generates an output voltage linearly proportional to the Centigrade temperature

$$V_{out} = 10^{-2} \cdot T$$

Thus in the specified conditions $V_{out} \in [0.1; 0.4]$, as done in the last section we will be using a differential amplifier to fit this interval in the *ADC*'s range.

3.3 DS18B20 ??(Este tem Dimensionamento?)

3.4 Relé de saída

4 Simulations

5 Implementation and Experimental Tests

6 Results Analysis

7 Conclusion